
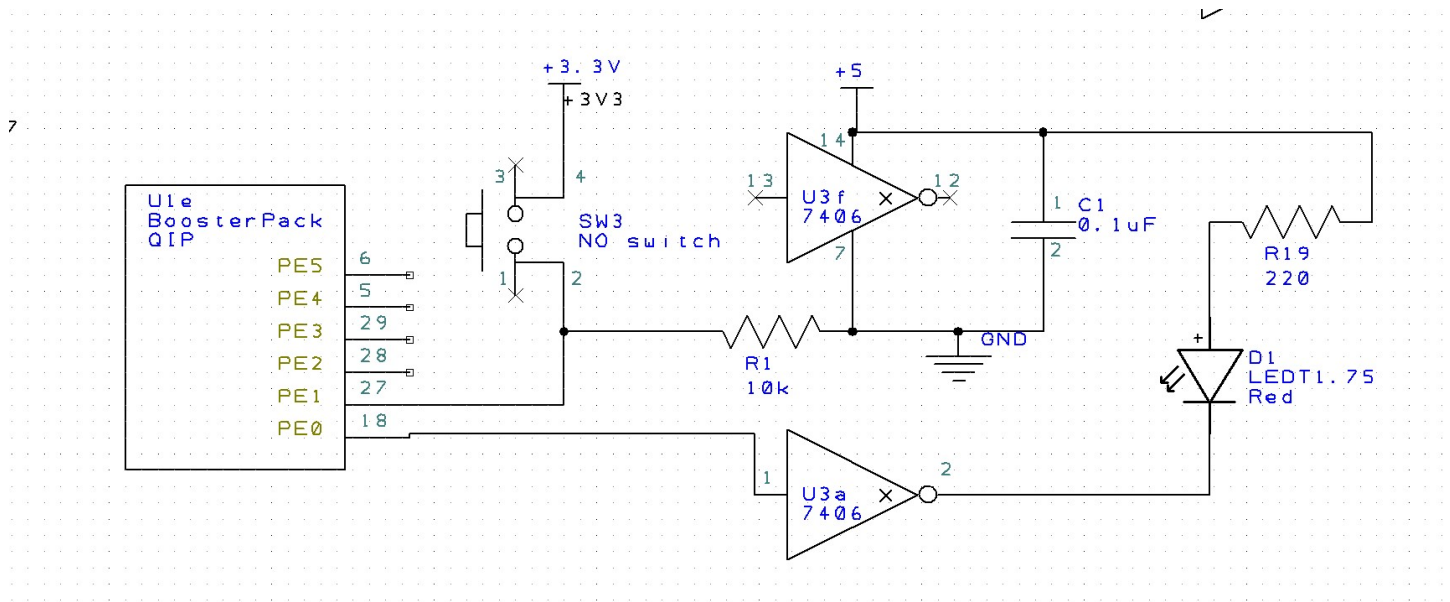


Circuit Diagram

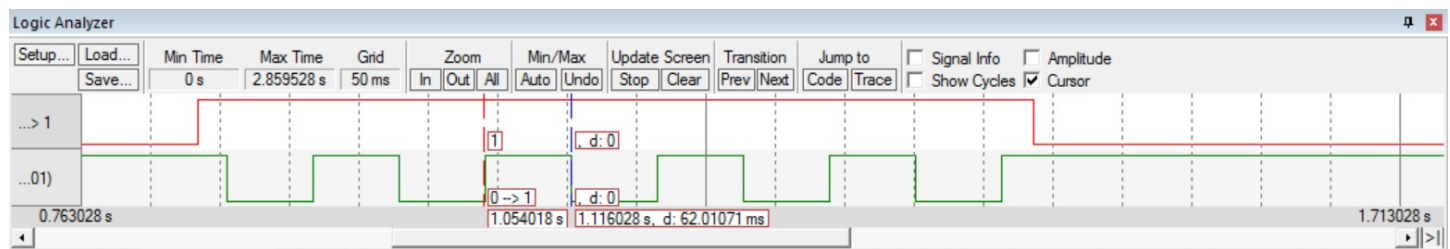

Simulator



Switch Measurements

Parameter	Value	Units	Conditions
Resistance of the 10kΩ resistor, R1	9.87k	ohms	with power off and disconnected from circuit (measured with ohmmeter)
Supply Voltage, $V_{+3.3}$	3.3	volts	Powered (measured with voltmeter)
Input Voltage, V_{PE1}	0	volts	Powered, but with switch not pressed (measured with voltmeter)

Resistor current	0	mA	Powered, but switch not pressed $I=V_{PEI}/R1$ (calculated and measured with an ammeter)
Input Voltage, V_{PEI}	3.3	volts	Powered and with switch pressed (measured with voltmeter)
Resistor current	0.33	mA	Powered and switch pressed $I=V_{PEI}/R1$ (calculated and measured with an ammeter)

LED Measurements

Row	Parameter	Value	Units	Conditions
1	Resistance of the 220 Ω resistor, R19	217	ohms	with power off and disconnected from circuit (measured with ohmmeter)
2	+5 V power supply V_{+5}	4.97	volts	(measured with voltmeter relative to ground, <i>notice that the +5V power is not exactly +5 volts</i>)
3	TM4C123 Output, V_{PE0} input to 7406	3.3	volts	with PE0 = 0 (measured with voltmeter relative to ground)
4	7406 Output, V_k LED k-	0.16	volts	with PE0 = 0 (measured with voltmeter relative to ground)
5	LED a+, V_{a+} Bottom side of R19	2.11	volts	with PE0 = 0 (measured with voltmeter relative to ground)
6	LED voltage	1.95	volts	calculated as $V_{a+} - V_k$
7	LED current	13	mA	calculated as $(V_{+5} - V_{a+})/R19$ and measured with an ammeter
8	TM4C123 Output, $V_{PE0'}$ input to 7406	2-1.3	volts	with PE0 = 1 (measured with voltmeter relative to ground)
9	7406 Output, V_k LED k-	2.3-1.4	volts	with PE0 = 1 (measured with voltmeter relative to ground)

10	LED a+, V_{a+} Bottom side of R19	3.8-3.1	volts	with PE0 = 1 (measured with voltmeter relative to ground)
11	LED voltage	1.4-1.1	volts	calculated as $V_{a+} - V_k$
12	LED current	5-8	mA	calculated as $(V_{+5} - V_{a+})/R19$ and measured with an ammeter

Assembly Code

```
,***** main.s *****
; Program written by: Chimezie Iwuanyanwu & Xinyuan Pan
; Date Created: 1/22/2016
; Last Modified: 2/20/2016
; Section: Wednesday 5-6
; Instructor: Ramesh Yerraballi
; Lab number: 3
; Brief description of the program
; If the switch is presses, the LED toggles at 8 Hz
; Hardware connections
; PE1 is switch input (1 means pressed, 0 means not pressed)
; PE0 is LED output (1 activates external LED on protoboard)
;Overall functionality of this system is the similar to Lab 2, with six changes:
;1- the pin to which we connect the switch is moved to PE1,
;2- you will have to remove the PUR initialization because pull up is no longer needed.
;3- the pin to which we connect the LED is moved to PE0,
;4- the switch is changed from negative to positive logic, and
;5- you should increase the delay so it flashes about 8 Hz.
;6- the LED should be on when the switch is not pressed
; Operation
; 1) Make PE0 an output and make PE1 an input.
; 2) The system starts with the LED on (make PE0 =1).
; 3) Wait about 62 ms
; 4) If the switch is pressed (PE1 is 1), then toggle the LED once, else turn the LED on.
; 5) Steps 3 and 4 are repeated over and over
```

```
GPIO_PORTE_DATA_R    EQU    0x400243FC
GPIO_PORTE_DIR_R     EQU    0x40024400
GPIO_PORTE_AFSEL_R   EQU    0x40024420
GPIO_PORTE_DEN_R     EQU    0x4002451C
GPIO_PORTE_AMSEL_R   EQU    0x40024528
GPIO_PORTE_PCTL_R    EQU    0x4002452C
SYSCTL_RCGCGPIO_R    EQU    0x400FE608
COUNT              EQU     1240000
    IMPORT TExaS_Init
    AREA    |.text|, CODE, READONLY, ALIGN=2
    THUMB
    EXPORT Start
```

Start

```
; TExaS_Init sets bus clock at 80 MHz
        BL TExaS_Init ; voltmeter, scope on PD3
; you initialize PE1 PE0
```

```
LDR R1, =SYSCTL_RCGCGPIO_R
LDR R0, [R1]
ORR R0, #0x10
STR R0, [R1]
NOP
NOP
```

```
LDR R1, =GPIO_PORTE_AMSEL_R
LDR R0, [R1]
AND R0, #0xFC
STR R0, [R1]
```

```
LDR R1, =GPIO_PORTE_PCTL_R
LDR R0, [R1]
AND R0, #0xFC
STR R0, [R1]
```

```
LDR R1, =GPIO_PORTE_DIR_R
LDR R0, [R1]
AND R0, #0xFC
ORR R0, #0x01
STR R0, [R1]
```

```
LDR R1, =GPIO_PORTE_AFSEL_R
LDR R0, [R1]
AND R0, #0xFC
STR R0, [R1]
```

```
LDR R1, =GPIO_PORTE_DEN_R
LDR R0, [R1]
ORR R0, #
STR R0, [R1]
```

B set_LED

CPSIE I

loop

BL delay

```
LDR R1, =GPIO_PORTE_DATA_R
LDR R0, [R1]
```

```
AND R2, #0
AND R2, R0, #0x02
LSR R2, #1
CMP R2, #1
```

BNE set_LED

```
EOR R3, R0, #0x01
STR R3, [R1]
```

```
B loop
```

```
set_LED
```

```
LDR R1, =GPIO_PORTC_DATA_R
LDR R0, [R1]
ORR R0, #0x01
STR R0, [R1]
```

```
B loop
```

```
delay
```

```
LDR R1, =COUNT
```

```
delay_loop
```

```
SUBS R1, #1
BNE delay_loop
BX LR
```

```
ALIGN
```

```
END
```